

Synchronous Switching Buck Regulator

Final Project (Jul-Nov 2018)

EE5325-Power Management Integrated Circuits

Subha Sarkar
Rupam K Chakraborty

Department of Electrical Engineering
Indian Institute of Technology, Madras

November 15, 2018

Contents

- 1 Introduction
- 2 Topology
- 3 Component Selection
- 4 Architecture
- 5 Design of Building Blocks
- 6 Novelty
- 7 Simulation Results
- 8 Performance Table

Introduction

Synchronous Switching DC-DC buck converter

Why switching ? Most of the switching regulators have lossless components which does not dissipate power so efficiency is better than linear counterpart.

Why Synchronous ? It almost eliminates the flyback-diode power loss (found in non-synchronous) by putting a low resistance path (NMOS) in parallel with the diode. The driver circuit now becomes complex (Dead time control).

What is buck ? It is topology in which output voltage is always lesser than the input voltage.

Topology

Voltage mode feed-forward topology [7]

Advantages

- ① Simplicity (Compensator design maybe complex)
- ② Devoid of dual feedback network (found in CMC)
- ③ No requirement of slope compensation
- ④ Supports high Dynamic range of output load current.

Disadvantages

- ① Slow line regulation (Solved using Feed-forward topology [6]).

Component Selection

Inductor Selection

For reduced RMS Loss, the inductor ripple is chosen to be 10% of Average(load) current (1A). So inductor ripple is chosen to be 100mA.


$$L = \frac{V_{in} \cdot D \cdot (1 - D)}{\Delta I \cdot F_{sw}} \implies L = 0.5625 \mu H \quad (1)$$

Capacitor Selection

To get minimum ripple we used following relation,

$$C = \frac{V_{in} \cdot D \cdot (1 - D)}{8 \cdot L \cdot \Delta V \cdot F_{sw}^2} \quad (2)$$

Architecture

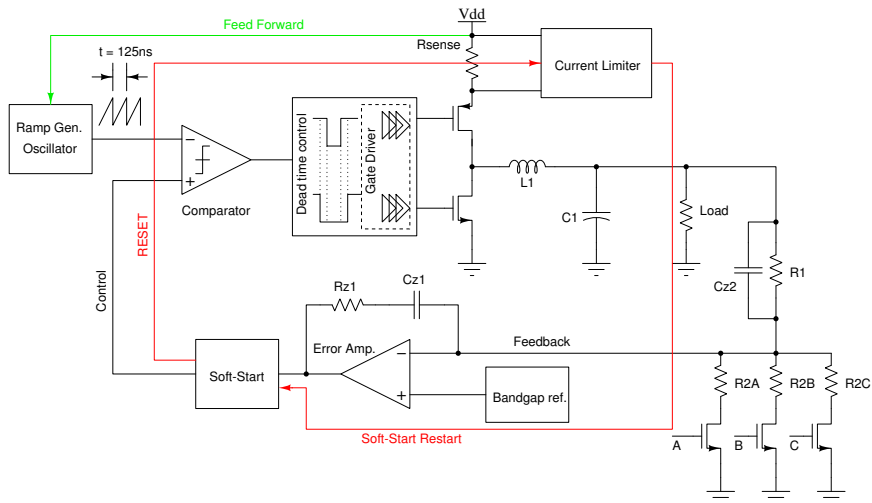

Power MOSFET sizing I

Given,

$$\eta = 90\% \quad (3)$$

$$R_{dcr} = 32m\Omega \quad (L = 0.47\mu H) \quad (4)$$

$$R_{sense} = 10m\Omega \quad (5)$$

$$P_{out}(\text{for worst case}) = 0.8W \quad (V_{out} = 0.8V) \quad (6)$$

$$I_{load}(\text{max.}) = 1A \quad (7)$$

$$\mu.C_{ox}/2 = 175.4\mu A/V^2, -35.6\mu A/V^2 \quad (8)$$

Assumptions

Switching loss = $0.3 \times$ Conduction Loss at 1A [9]

$$R_{PMOS} = R_{NMOS} = R_{ds}$$

Power MOSFET sizing II

Therefore Conduction loss, $P_{conduction}$

$$P_{conduction} = I_{load}^2 \cdot (R_{dcr} + R_{ds} + R_{sense}) = \left(\frac{1}{\eta} - 1 \right) \cdot \frac{P_{out}}{1.3} \quad (9)$$

$$\implies R_{ds} = 68.37 m\Omega - 32 m\Omega - 10 m\Omega = 26.37 m\Omega \quad (10)$$

$$\left(\frac{W}{L} \right) = \frac{1}{\mu \cdot C_{ox} \cdot (V_{gs} - V_t) \cdot R_{MOS}} \quad (11)$$

$$\implies \left(\frac{W}{L} \right)_n = 83799 \implies W_n = 15.08 mm \quad (12)$$

$$\implies \left(\frac{W}{L} \right)_p = 412876 \implies W_p = 74.33 mm \quad (13)$$

Comparator

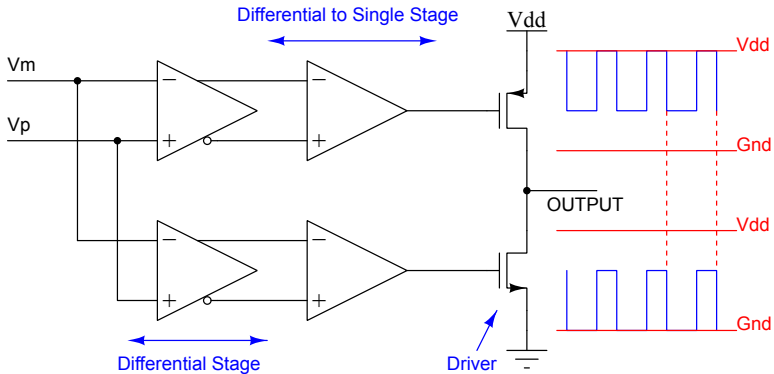


Figure: Comparator block diagram [5]

Oscillator & Ramp Generator

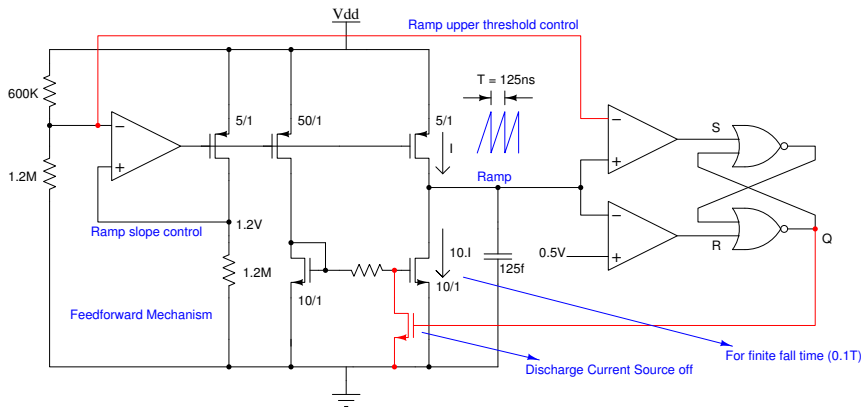


Figure: Oscillator & Ramp Generator[3]

Soft Start

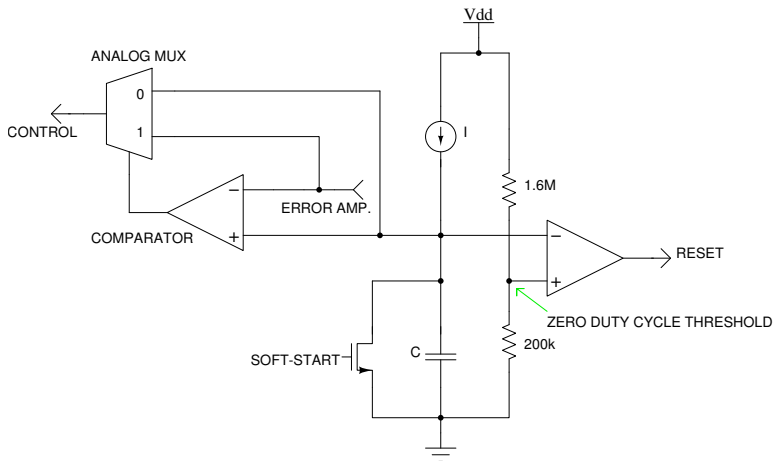


Figure: Soft Start

Current Limiter

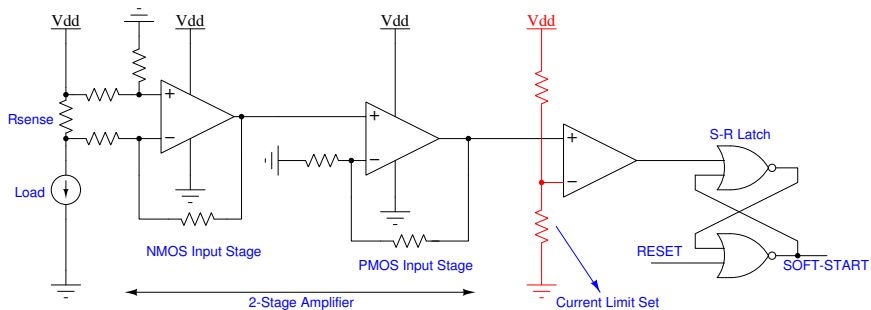


Figure: High Side Current Sensor[11][4] and Short circuit limiter with Auto-Wake up (Hicup) Mode

Bandgap Reference

 


Figure: Current mode Sub-1V bandgap reference[1]

Amplifier

 


Figure: Schematic of Amplifiers used.

Dead time generator & Gate drivers

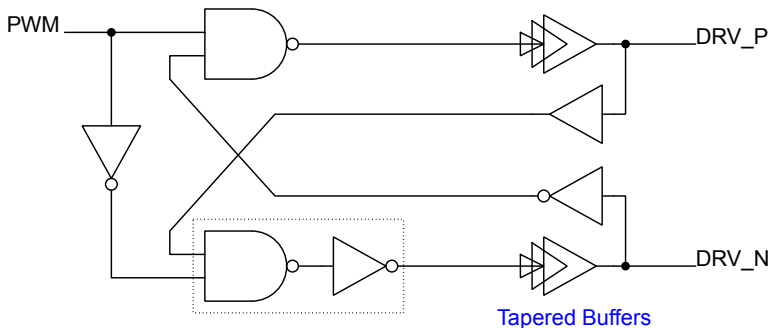


Figure: Gate drivers[2] and Dead time generator; Scaling factor of tapered buffers = 6 and No. of stages = 4

Novelty

- 1 **Softstart circuit [8] [10]** - It limits Inrush Current along with Duty cycle continuity which reduces the peaking.
- 2 **Peak Current Limit** - It restarts the soft-start cycle to slowly increase the output voltage & checks if the short still exists or not. High side sensing [11] is implemented for this purpose.
- 3 **Startup circuit of Bandgap reference [1]** - A RC Circuit based Startup Circuit which consumes no current at steady state.
- 4 **Oscillator & Feedforward** - It improves the line regulation speed [7] in voltage mode control.

General Results

Parameters	Values
Input voltage Range	1.7 - 1.8V
Output Range	0.5 - 1.6V
Load Current Range	1mA-1A
Switching Frequency	7.98MHz
Inductor	0.47u
Capacitor	11u

Table: General Results for all upcoming slides

Bandgap Reference

 


Figure: Bandgap reference temperature curve

Compensator

 


Figure: Compensator Frequency response

Simulation Results I

 


Figure: Line transient for rising VDD, $V_{out} = 1.5V$

Simulation Results II

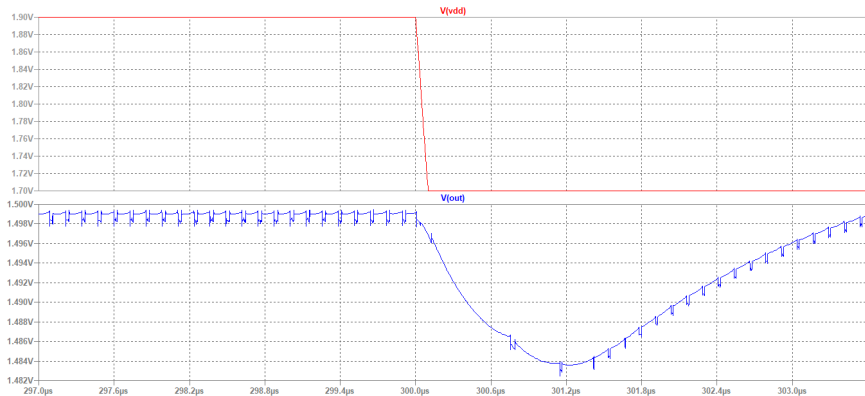


Figure: Line transient for falling VDD, $V_{out} = 1.5\text{V}$

Simulation Results III

 


Figure: Load Transient Overshoot response for $V_{out} = 1.5V$

Simulation Results IV

 


Figure: Load Transient Undershoot response for $V_{out} = 1.5\text{V}$

Simulation Results V

 


Figure: Output ripple for $V_{out} = 1.5\text{V}$

Performance Table - $V_{out} = 1.5V$

Parameters	Results/Values (1mA)	Results/Values (1A)
Settling time (PWM Cycles)	22	
DC output voltage inaccuracy	0.0533%	0.0333%
Overshoot (Load Transient)	0.988%	
Undershoot (Load Transient)	4.193%	
Overshoot (Line Transient)	0.978%	1.298%
Undershoot (Line Transient)	1.064%	1.113%
Efficiency (%)	13.6%	93.79%
Output ripple voltage (PWM)	1.42mVpp	1.53mVpp
FOM2	1.021×10^{-5}	

Table: Performance parameters for $V_{out} = 1.5V$

Simulation Results I

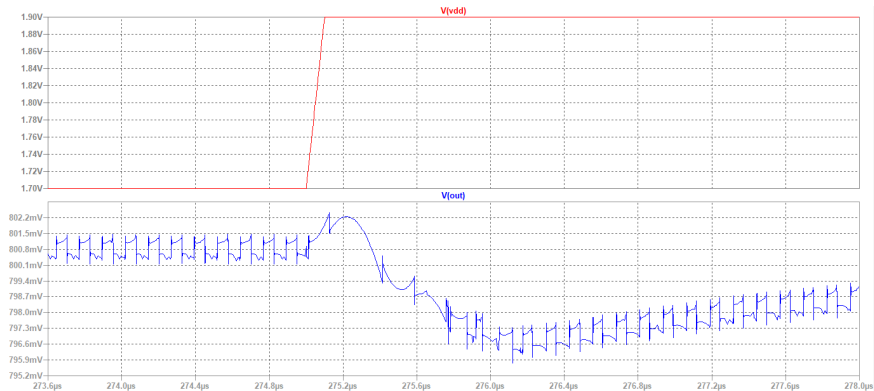


Figure: Line transient for rising VDD, $V_{out} = 0.8V$

Simulation Results II

 


Figure: Line transient for falling VDD, $V_{out} = 0.8\text{V}$

Simulation Results III

 


Figure: Load Transient Overshoot response for $V_{out} = 0.8V$

Simulation Results IV

 


Figure: Load Transient Undershoot response for $V_{out} = 0.8\text{V}$

Simulation Results V

 


Figure: Output ripple for $V_{out} = 0.8V$

Performance Table - $V_{out} = 0.8V$

Parameters	Results/Values (1mA)	Results/Values (1A)
Settling time (PWM Cycles)	14	
DC output voltage accuracy	0.016%	0.04%
Overshoot (Load Transient)	2.880%	
Undershoot (Load Transient)	3.036%	
Overshoot (Line Transient)	0.388%	0.151%
Undershoot (Line Transient)	0.145%	0.257%
Efficiency (%)	9.8%	82.61%
Output ripple voltage (PWM)	1.39mVpp	1.53mVpp
FOM2	2.86×10^{-5}	

Table: Performance parameters for $V_{out} = 0.8V$

Simulation Results I

 


Figure: Line transient for rising VDD, $V_{out} = 1.2V$

Simulation Results II

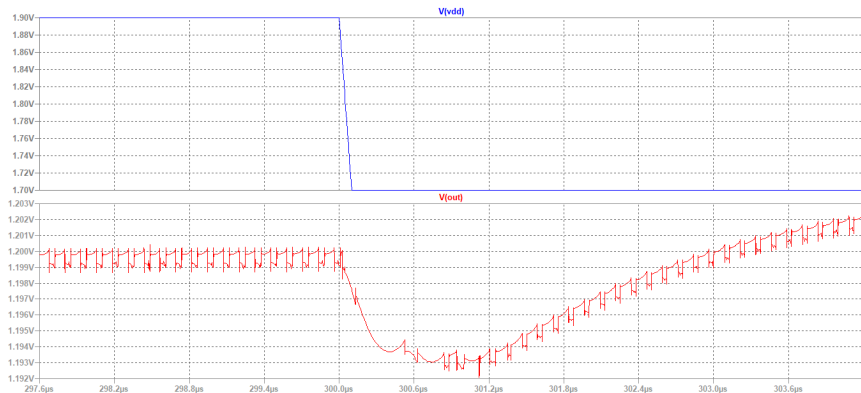


Figure: Line transient for falling VDD, $V_{out} = 1.2V$

Simulation Results III

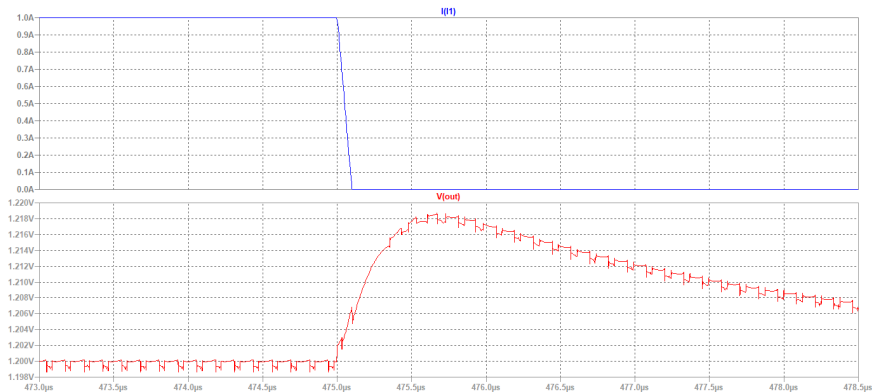


Figure: Load Transient Overshoot response for $V_{out} = 1.2\text{V}$

Simulation Results IV

 


Figure: Load Transient Undershoot response for $V_{out} = 1.2\text{V}$

Simulation Results V

 


Figure: Output ripple for $V_{out} = 1.2V$

Performance Table - $V_{out} = 1.2V$

Parameters	Results/Values (1mA)	Results/Values (1A)
Settling time (PWM Cycles)	15	
DC output voltage inaccuracy	0.025%	0.05%
Overshoot (Load Transient)	1.586%	
Undershoot (Load Transient)	2.986%	
Overshoot (Line Transient)	0.589%	0.899%
Undershoot (Line Transient)	0.490%	0.547%
Efficiency (%)	11.76%	92.55%
Output ripple voltage (PWM)	916 μ Vpp	1.53mVpp
FOM2	2.187×10^{-5}	

Table: Performance parameters for $V_{out} = 1.2V$

Short Circuit Protection - Simulation

 


Figure: Transient response with Auto-Start up (Hicup mode)

References I

- [1] H. Banba et al. “A CMOS bandgap reference circuit with sub-1-V operation”. In: *IEEE Journal of Solid-State Circuits* 34.5 (May 1999), pp. 670–674. ISSN: 0018-9200. DOI: 10.1109/4.760378.
- [2] Brian S Cherkauer and Eby G Friedman. “A unified design methodology for CMOS tapered buffers”. In: *IEEE Transactions on Very Large Scale Integration (VLSI) Systems* 1 (1995), pp. 99–111.
- [3] H Pooya Forghani-Zadeh and Gabriel A Rincón-Mora. “Low-power CMOS ramp generator circuit for DC-DC converters”. In: *journal of low power electronics* 2.3 (2006), pp. 437–441.

References II

- [4] Hassan Pooya Forghani-Zadeh and Gabriel A Rincon-Mora. “Current-sensing techniques for DC-DC converters”. In: *Circuits and Systems, 2002. MWSCAS-2002. The 2002 45th Midwest Symposium on*. Vol. 2. IEEE. 2002, pp. II-II.
- [5] Analog Devices Inc., ed. *AD8469, Fast, Rail-to-Rail, Low Power, 2.5 V to 5.5 V, Single-Supply TTL/CMOS Comparator*.
- [6] Robert A. Mammano. *Applying the UCC3570 Voltage-Mode PWM Controller to both off-line and DC/DC Converter Designs*. Application Note. Texas Instruments, 1999.
- [7] Robert A. Mammano. *Switching Power Supply Topology Voltage Mode vs. Current Mode*. Design Note. Texas Instruments, 1999.

References III

- [8] *Selecting the Right CMOS Analog Switch*. URL: <https://www.maximintegrated.com/en/app-notes/index.mvp/id/5299>.
- [9] *Switching Regulator IC Series Series, Efficiency of Buck Converter, Pg. 12/15*. Application Note. Rohm Semiconductors.
- [10] Linear Technology, ed. *LT3479 - 3A, Full Featured DC/DC Converter with Soft-Start and Inrush Current Protection*.
- [11] Michael Stokowski Tim Regan Jon Munson Greg Zimmer. *Current Sense Circuit Collection*. Application Note. Linear Technology Inc.